

A
Seminar report
on
Low Cost Automatic

Submitted in partial fulfillment of the requirement for the award of degree
of Electronics

SUBMITTED TO:

www.studymafia.org

SUBMITTED BY:

www.studymafia.org

Preface

I have made this report file on the topic **Low Cost Automatic**. I have tried my best to elucidate all the relevant detail to the topic to be included in the report. While in the beginning I have tried to give a general view about this topic.

My efforts and wholehearted co-corporation of each and everyone has ended on a successful note. I express my sincere gratitude towho assisting me throughout the prepration of this topic. I thank him for providing me the reinforcement, confidence and most importantly the track for the topic whenever I needed it.

www.studymafia.org

LOW COST AUTOMATIC


CONTENTS

1. INTRODUCTION
2. OBJECTIVE
3. BLOCK DIAGRAM
4. CIRCUIT DIAGRAM
5. WORKING
6. COMPARITIVE STUDY OF CIRCUIT WITH AND WITHOUT PWM
7. FEATURES
8. ADVANTAGES AND DISADVANTAGES OF LED
- COMPARISON OF LED LAMPS WITH OTHER LIGHTINGTECHNOLOGIES
9. CONCLUSION
- 10.FUTURE SCOPE
11. REFERENCES

INTRODUCTION

- Growing demand for the saving of electricity.
- Failure in power supply causes difficulty and inconvenience.
- An automatic emergency lamp that uses LED .
- Highly bright due to use of white LEDs.
- Turns on when mains supply fails ,turns off when power resumes.
- Has own battery charger –stops charging automatically when fully charged.
- This project aims to develop most power efficient and user friendly product.

CIRCUIT DIAGRAM

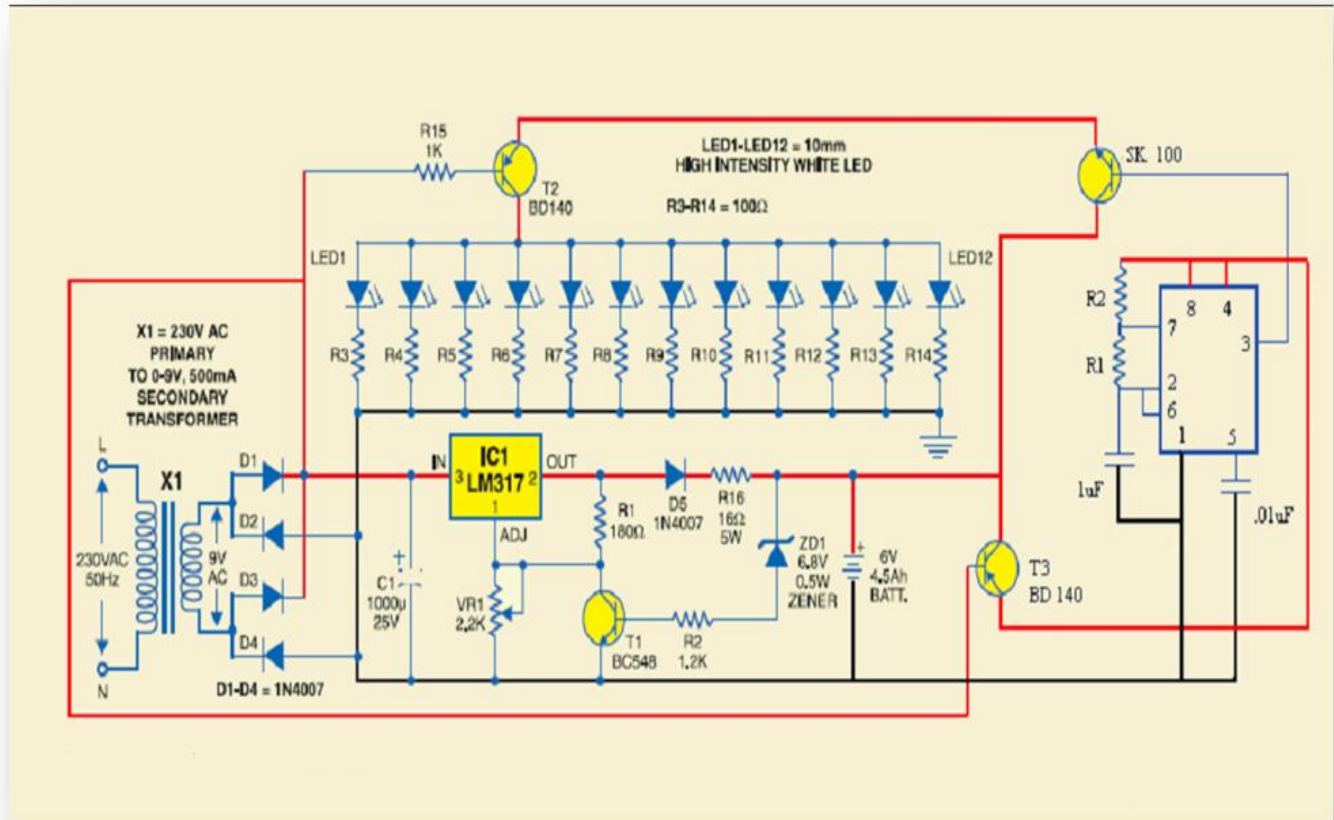

WORKING

The circuit has three sections:

- **The charger power supply section:**
 - Transformer: steps down(9V,500mA).
 - Bridge rectifier: rectifies transformer output.
 - LM317: voltage regulation.
 - Battery: provides supply when mains fails.
 - Zener diode: conducts when battery crosses its capacity.
- **555 timer section:**
 - Control the LED section by PWM.
- **LED driver section:**
 - Build around BD 140.
 - 12 white LEDs connected in parallel.
 - LED section glows when mains fails.
 - Made to blink using astable operation of 555.
 - Appear fulltime ON due to persistence of vision

ADVANTAGES AND DISADVANTAGES OF LED

- Efficiency: more light per watt than incandescent bulbs.
- Color: can emit of an intended color without use of color filters.
- Size: very small.
- On/off time: light up very quickly.
- cycling: can be subjected to frequent on-off cycling.
- Dimming: can be dimmed by PWM.

- Slow failure: mostly fail by dimming over time, rather than abrupt burn-out of incandescent bulbs.
- Life time: long useful life time.
- Toxicity: LEDs do not contain mercury, unlike fluorescent lamps.

CONCLUSION

- The project was concluded to be innovative for the improvement of day today life.
- Device also adds a new look to the traditional lamps.
- The use of PWM helps us to reduce the wastage of energy.
- The cost of implementing this circuit is also very less - an added advantage in using this circuit.

FUTURE SCOPE

- We can again modernize this project using PWM.
- It is expected that with additional development and growing researches, the PWM will gain more popularity and the cost of these bulbs will eventually decline.
- This project can be adopted for mass production as cheap and efficient method.



REFERENCES

- www.studymafia.org
- www.wikipedia.com
- www.google.com

www.studymafia.org